
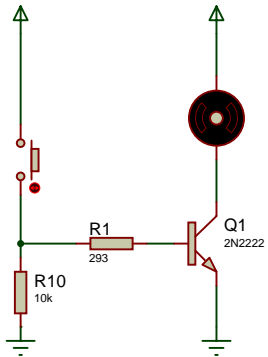


One Direction Motor Circuits


NPN Transistor (2N2222)
Active HIGH

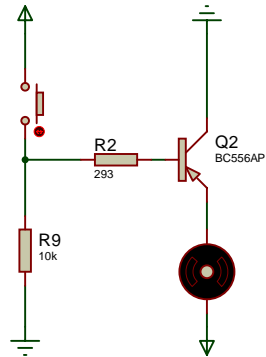


PNP Transistor (BC556)
Active LOW




Relay 5V, 47 Res + Motor (Driving)

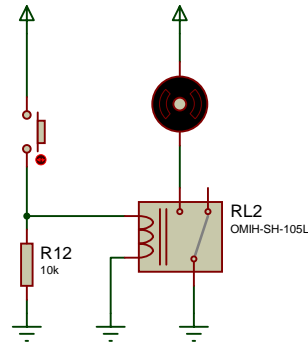


Relay 5V, 47 Res + NPN trans
Active HIGH

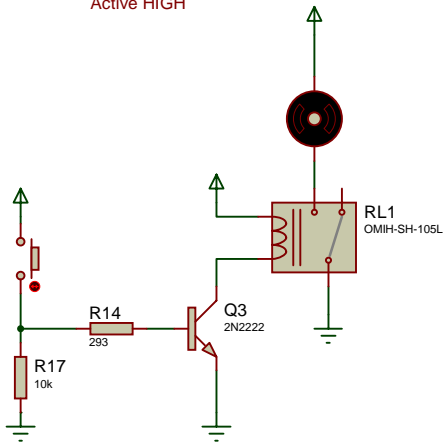

Relay 5V, 47 Res + PNP trans
Active LOW

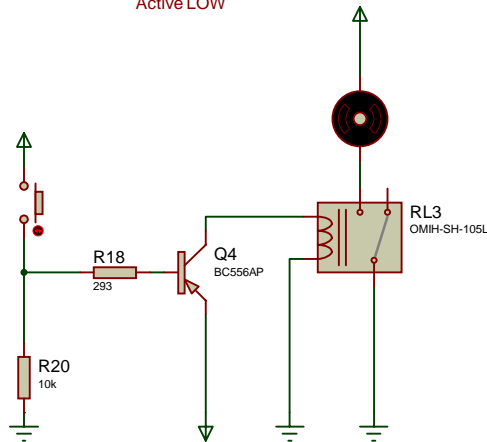

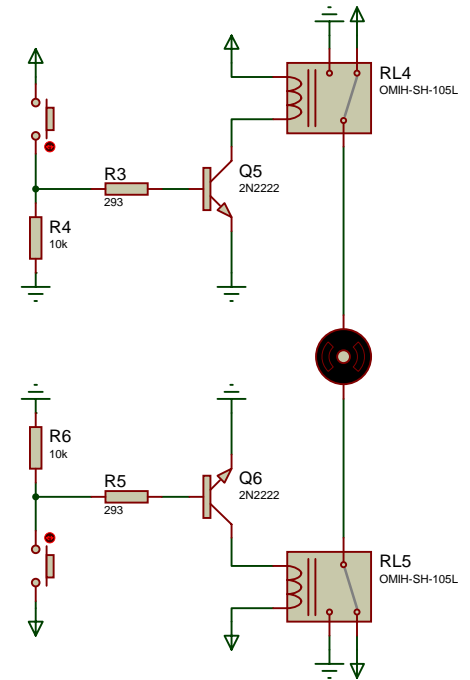**2 Direction Motor Using
2 Relays, 2 NPN trans**



2 Direction Motor Using H Bridge Concept (2 NPN, 2PNP)

